


CSUS CPE166 Dummy2 Exercise

Student Name: Shammah Thao

You need to upload the solution in multi-page PDF or WORD file format on the canvas course website.

You must write down your name on your solution sheets.

 1. Complete the **Verilog** HDL design for the following finite state machine.



```
module fms ( reset, clk, a, y );

input  reset, clk, a;

output y;

parameter s0=0,s1=1,s2=2,s3=3,s4=4;
reg[2:0] cu,ns;

always @(posedge clk)

begin
if(rst)
cs <= s0;
else cs <= ns;
end

always@(a,cs)
begin
case(cs)
so: begin
if(in)
begin
ns<= s1;
y<=0;
end
end
end
```

```

        else
        begin
        ns<=s0;
        y<=0;
        end
    end

s1:begin
    if(in)
    begin
    ns<= s2;
    y<=0;
    end
else
    begin
    ns<=s0;
    y<=0;
    end
end

s2:begin
    if(in)
    begin
    ns<= s2;
    y<=0;
    end
else
    begin
    ns<=s3;
    y<=0;
    end
end


s3:begin
    if(in)
    begin
    ns<= s4;
    y<=0;
    end
else
    begin
    ns<=s0;
    y<=0;
    end
end

s4:begin
    if(in)

```

```
        begin
        ns<= s2;
        y<=1;
        end
else
        begin
        ns<=s0;
        y<=0;
        end
end

 default :begin
        if(in)
        begin
        ns<= s0;
        y<=0;
        end
endcase
endmodule
```



// Continue your Verilog design on this page.

.....

2. Fill out 6 blanks in the following Verilog design with the given circuit schematic.

```


module ex2(D, E, F, G, H, Y);
input  D, E, F, G, H;
output Y;
reg    M, N, Y;
always@(D or E or F or G or H)
begin
    M = subcir ( __F__, __E__, __D__);

    N = subcir ( __F__, __G__, __H__);

    Y = M | N;
end

function subcir;
input A, B, C;
reg P;
begin
    P = A & B;
    subcir = P | C;
end
endfunction
endmodule

```

 

VHDL Exercises are for questions below.

Note: VHDL is not case sensitive.

3. Use when ... else statement to design 4 to 1 multiplexer.

Library ieee;

Use ____iee.std_logic_1164.all_____;

Entity mux4to1 is

Port (d0, d1, d2, d3: in std_logic;

S: in ____std_logic_____ ;

Y out ____std_logic_____);

End mux4to1;

Architecture beh1 of mux4to1 is

Begin

Y <= d0 when __S= '0' _____ else

d1 when __S= '1' _____ else

d2 when _____S= '1' _____ else

d3;

End beh1;

4. Use with ... select statement to design 4 to 1 multiplexer.
(Entity part is same with that used in question 3).

Architecture beh2 of mux4to1 is

Begin

With S select

Y <= d0 when ____S='0' _____ ,

d1 when _____S='1' _____ ,

d2 when _____S='1' _____ ,

d3 when others;

End beh2;

5. Use if ... else statement to design 4 to 1 multiplexer.
(Entity part is same with that used in question 3).

Architecture beh3 of mux4to1 is

Begin

Process(d0, d1, d2, d3, S)

begin

if (__S='0'_____) then

Y <= d0;

elsif (_____S='1'_____) then

Y <= d1;

elsif (_____S='1'_____) then

Y <= d2;

else


Y <= d3;

end if;

End process;

End beh3;

 6. Complete the VHDL statements to describe waveforms A and B.



A <= '0', '1' after _10_ ns, '0' after _20_ ns, '1' after _50_ ns, '0' after _60_ ns;

Process

Begin

B <= '0';

Wait for _20_ ns;

B <= '1';

Wait for _10_ ns;

B <= '0';

Wait for _20_ ns;

B <= '1';

Wait for _30_ ns;

Wait;

End process;