

CPE 166 Advance Logic Design

Lab Section 2

Lab 4

Shammah Thao

12/1/20

Table of Contents

Introduction	3
Part 1: SRAM Design.....	3
Design Purpose	3
Verilog Data:	3
Verilog Code.....	4
Results Discussion	6
Part 2,3,4: Simplified Microprocessor Design.....	6
Design Purpose	6
Verilog Data:	8
Verilog Code.....	10
Results Discussion	17
Conclusion.....	17

Introduction:

In this 4-part lab we were to design a SRAM design that reads and write data and a simplified Microprocessor. A SRAM is a type of random-access memory that uses latching circuitry to store each bit. It loses its data every time the power is lost making it faster than DRAM. A microprocessor, on the other hand, is a computer processor that is implemented on a single integrated circuit of MOSFET construction. The microprocessor is a multipurpose, clock-driven, register-based, digital integrated circuit that accepts binary data as input, processes it according to instructions stored in its memory, and provides results (also in binary form) as output. Microprocessors contain both combinational logic and sequential digital logic. Microprocessors operate on numbers and symbols represented in the binary number system.

Part 1: SRAM

Design Purpose:

The purpose of this part of the lab is to write in Verilog a SRAM that could read and write in 4 bits in a 32-address location. The coding would include 2 parts, the RAM and the memory which was given to us and we would have to compete.

Verilog Design:

WE	CS	OE	Function
X	L	X	High-z
L	H	L	High-z
L	H	H	Read Data
H	H	X	Write Data

Figure 1: SRAM Function Table

Verilog Code:

Mem_fsm

Source Code	Testbench
<pre>`timescale 1ns / 1ps module mem_fsm(clk,reset,address,data,cs,we,oe);input clk, reset; output [3:0] address; inout [3:0] data; output cs, we, oe; reg cs, we, oe; reg [5:0] address; reg [3:0] data_reg; reg [2:0] state; parameter idle = 3'b000, s1= 3'b001, s2= 3'b010, s3=3'b011; assign data = data_reg; always@(posedge clk or posedge reset) begin if (reset) begin state <= idle; address <= 0; end else case (state) idle: begin state <= s1; address <= 0; end s1: begin state <= s2; address <= 0; end s2: begin if(address == 32) begin state <= s3; end else begin address <= address + 1; state <= s2; end end end</pre>	

<pre>end s3: begin if(address == 0) begin state <= s1; end else begin address <= address - 1; state <= s3; end end default: begin state <= idle; address <= 0; end endcase end always@(state) begin case (state) idle: begin cs = 0; we = 0; oe = 0; data_reg = 4'bZZZZ; end s1: begin cs = 1; we = 1; oe = 0; data_reg = 4'b1010; end s2: begin cs = 1; we = 1; oe = 0; data_reg = 4'b1010; end s3: begin cs = 1; we = 0; oe = 1; end default: begin</pre>	
--	--


<pre> cs = 0; we = 0; oe = 0; data_reg = 4'b1010; end endcase end endmodule </pre>	
--	--

Ram

Source Code	Test bench
<pre> module SRAM (address, data, cs, we, oe); input cs, we, oe; input [5:0] address; inout [7:0] data; reg [7:0] data_out; reg [7:0] mem [0:1023]; assign data = (cs && oe && !we) ? data_out : 8'bzzzzzzzz; always @ (cs or we or data or address) if (cs && we) mem [address] = data; always @ (cs or we or data or address or data) begin if (cs && !we && oe) data_out = mem[address]; end endmodule </pre>	

Top

Source Code	Testbench
<pre> module top(clk, reset, address, data, cs, we, oe); input clk, reset, cs, we, oe; output [7:0] address; inout [3:0] data; mem_fsm g1(.clk(clk), .reset(reset), .address(address), .data(data), .cs(cs), .we(we), .oe(oe)); </pre>	<pre> module top_tb(); reg clk, reset; wire [5:0] address; wire [3:0] data; top uut(.clk(clk),.reset(reset),.address(address),.data(data)); always begin #5 clk = ~clk; end initial begin </pre>

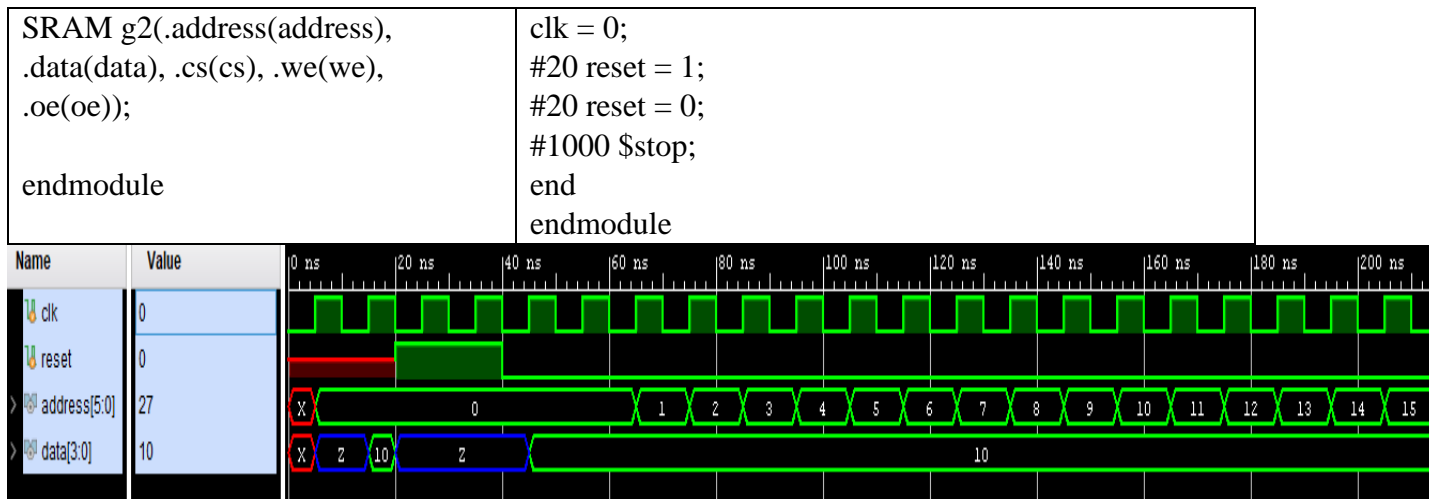

Result Discussion:

The result came out as intended. Getting the solution was easier than expected. I assumed we were supposed to add more states to the mem_fsm which made it more complicated than it was. The shorter the code was the easier it was since it was just a simply fill in the blank. It was a good reminder of the Verilog coding along with fsm.

Part 2,3,4: Simplified Microprocessor Design

Design Purpose:

The purpose of this was to make a simplified microprocessor diagram with two input into a fsm which leads to a datapath that accepts an additional 4 inputs, giving us 3 outputs in arrays. There was about 3 part to this lab which are required to be join together in a hierarchy format.

$$R2 = M0 + (\text{not } M1) + \text{Cin}$$

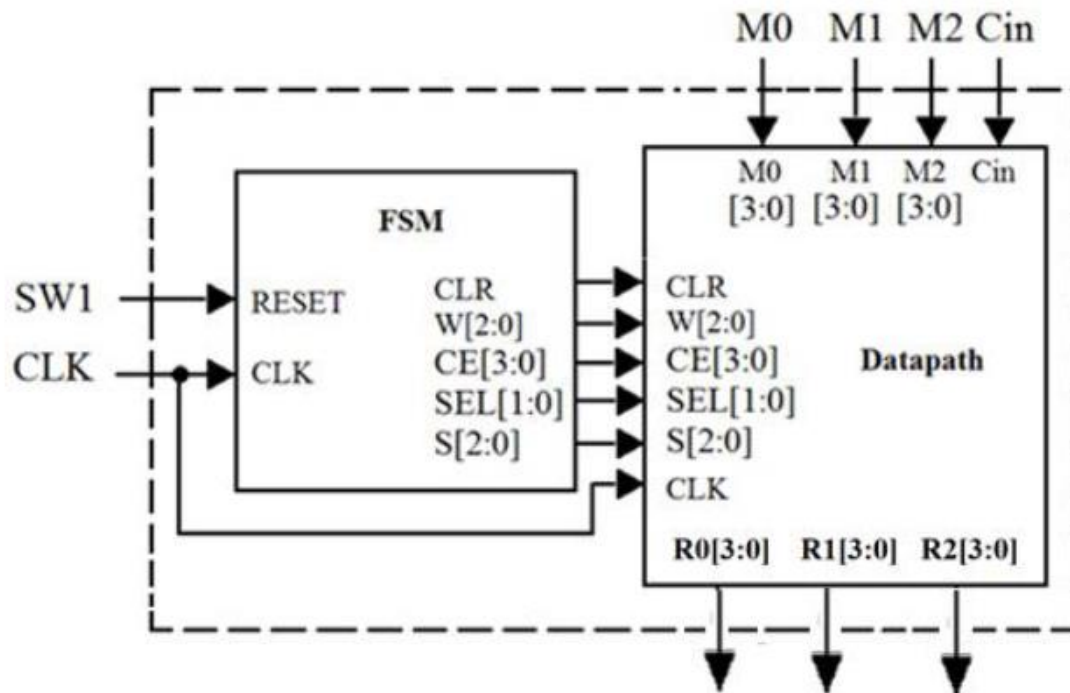


Figure 4-1. Simplified microprocessor block diagram

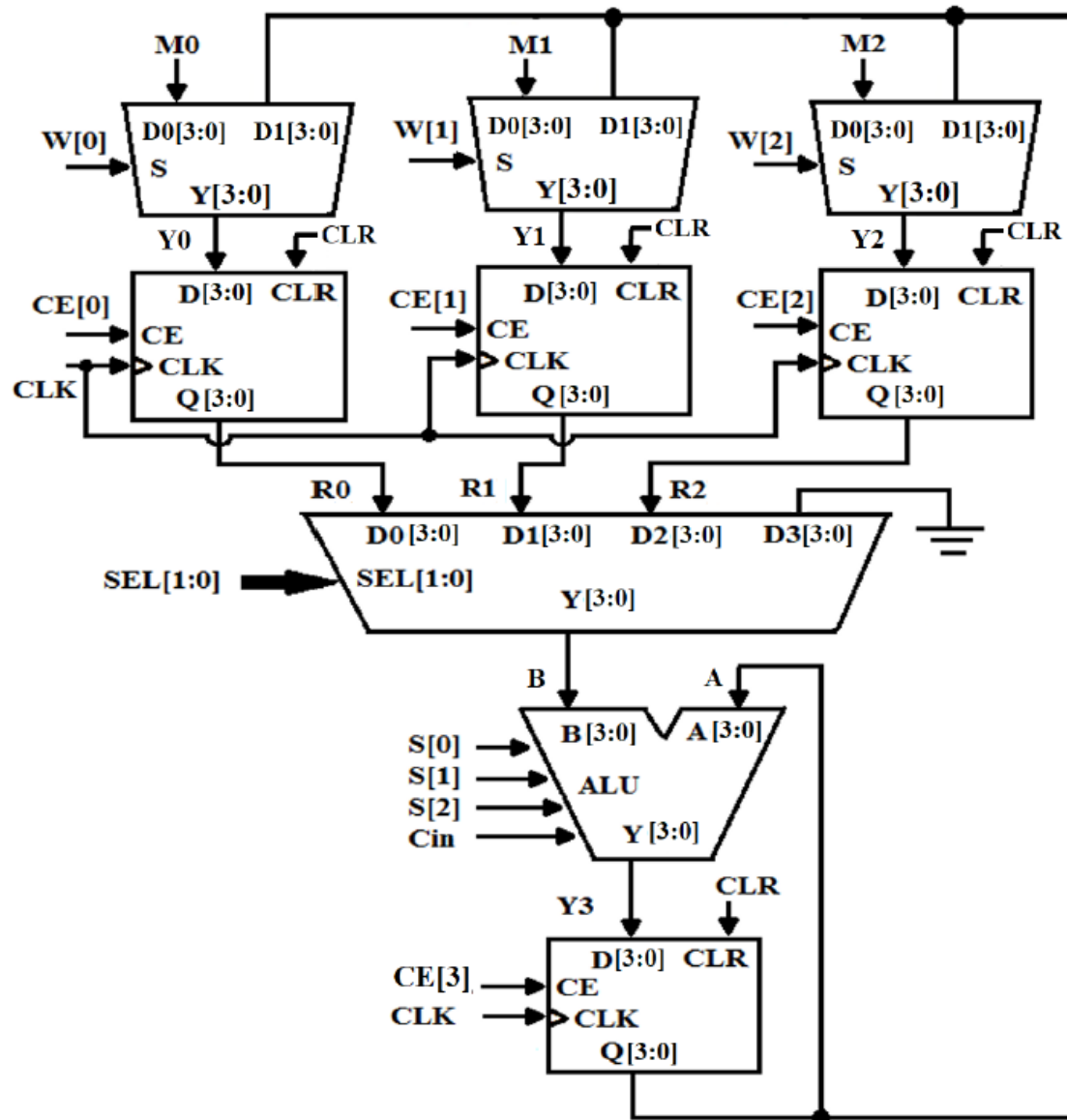


Table 4-1. ALU truth table

S[2]	S[1]	S[0]	ALU Output F
0	0	0	$F = A + B + C_{in}$
0	0	1	$F = A + B' + C_{in}$
0	1	0	$F = B$
0	1	1	$F = A$
1	0	0	$F = A \text{ AND } B$
1	0	1	$F = A \text{ OR } B$
1	1	0	$F = A'$
1	1	1	$F = A \text{ XOR } B$

 



Figure 4-3. Simplified microprocessor control path block diagram

Verilog Code:

Mux 2 to 1


Source Code	Testbench
<pre> module mux2to1(d0, d1, s, y); input[3:0] d0, d1; input s; output reg[3:0] y; always@(d0 or d1 or s) begin if(s) y = d1; else y = d0; end </pre>	<pre> module mux2to1_tb; reg[3:0] d0, d1; reg s; wire[3:0] y; mux2to1 u1(d0, d1, s, y); initial begin d1 = 0; d0 = 0; s = 0; end </pre>

<pre> end endmodule </pre>	<pre> #10 d1 = 0; d0 = 0; s = 1; #10 d1 = 0; d0 = 1; s = 0; #10 d1 = 0; d0 = 1; s = 1; #10 d1 = 1; d0 = 0; s = 0; #10 d1 = 1; d0 = 0; s = 1; #10 d1 = 1; d0 = 1; s = 0; #10 d1 = 1; d0 = 1; s = 1; #10 \$stop; end endmodule </pre>
----------------------------	---

 

Mux4to1

<pre> Source Code module mux4to1(d0, d1, d2, d3, sel, y); input[3:0] d0,d1,d2,d3; input[1:0] sel; output reg[3:0] y; always @(d0 or d1 or d2 or d3 or sel) begin case (sel) 2'b00: y = d0; 2'b01: y = d1; 2'b10: y = d2; 2'b11: y = d3; endcase end endmodule </pre>	<pre> Testbench module mux4to1_tb; reg[3:0] d0, d1, d2, d3; reg[1:0] sel; wire[3:0] y; mux4to1 u1(d0, d1, d2, d3, sel, y); initial begin d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b00; #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b01; #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b10; #10 d0 = 0; d1 = 1; d2 = 2; d3 = 3; sel = 2'b11; #10 \$stop; end endmodule </pre>
--	---

 

Diff

Source Code	Testbench												
<pre> module diff (clk, clr, d, q, ce); input[3:0] d; input clk, ce, clr; output reg[3:0] q; always@(posedge clr or posedge clk) begin if(clr) q <= 0; else if(ce) q <= d; end endmodule </pre>	<pre> module diff_tb; reg[3:0] d; reg clk, clr, ce; wire[3:0] q; diff u1(clk, clr, d, q, ce); initial clk = 0; always #10 clk = ~clk; initial begin clr = 1; d = 1; ce = 1; #20 clr = 0; #20 ce = 0; #40 \$stop; end endmodule </pre>												
<table border="1"> <thead> <tr> <th>Name</th><th>Value</th></tr> </thead> <tbody> <tr> <td>d[3:0]</td><td>1</td></tr> <tr> <td>clk</td><td>1</td></tr> <tr> <td>clr</td><td>0</td></tr> <tr> <td>ce</td><td>0</td></tr> <tr> <td>q[3:0]</td><td>1</td></tr> </tbody> </table>	Name	Value	d[3:0]	1	clk	1	clr	0	ce	0	q[3:0]	1	
Name	Value												
d[3:0]	1												
clk	1												
clr	0												
ce	0												
q[3:0]	1												


ALU

Source Code	Testbench
<pre> module alu(a, b, s, cin, y); input[3:0] a, b; input[2:0] s; input cin; output reg[3:0] y; always@(a or b or s or cin or y) begin case(s) 3'b000: y = a + b + cin; 3'b001: y = a + ~b + cin; 3'b010: y = b; 3'b011: y = a; 3'b100: y = a & b; 3'b101: y = a b; 3'b110: y = ~a; 3'b111: y = a ^ b; endcase end endmodule </pre>	<pre> module alu_tb; reg[3:0] a, b; reg[2:0] s; reg cin; wire[3:0] y; alu u1(a, b, s, cin, y); initial begin s = 0; a = 1; b = 2; cin = 1; #10 s = 1; a = 1; b = 0; cin = 1; #10 s = 2; a = 1; b = 0; cin = 1; #10 s = 3; a = 1; b = 0; cin = 1; #10 s = 4; a = 1; b = 0; cin = 1; #10 s = 5; a = 1; b = 0; cin = 1; #10 s = 6; a = 1; b = 0; cin = 1; #10 s = 7; a = 1; b = 0; cin = 1; #10 \$stop; end endmodule </pre>

Name	Value	0 ns	10 ns	20 ns	30 ns	40 ns	50 ns	60 ns	70 ns
a[3:0]	1					1			
b[3:0]	0	2				0			
s[2:0]	7	0	1	2	3	4	5	6	7
cin	1								
y[3:0]	1	4	1	0	1	0	1	e	1

Datapath

Source Code	Testbench
<pre> module dp(m0, m1, m2, cin, clr, w, ce, sel, s, clk, r0, r1, r2); input clk, clr, cin; input[3:0] m0,m1,m2,ce; input[2:0] w, s; input[1:0] sel; output[3:0] r0, r1, r2; wire [3:0] y0, y1, y2, y3, a, b; mux2to1 g1(.d0(m0),.d1(a),.s(w[0]),.y(y0)); mux2to1 g2(.d0(m1),.d1(a),.s(w[1]),.y(y1)); mux2to1 g3(.d0(m2),.d1(a),.s(w[2]),.y(y2)); diff d1(.clk(clk),.clr(clr),.ce(ce[0]),.d(y0),.q(r0)); diff d2(.clk(clk),.clr(clr),.ce(ce[1]),.d(y1),.q(r1)); diff d3(.clk(clk),.clr(clr),.ce(ce[2]),.d(y2),.q(r2)); diff d4(.clk(clk),.clr(clr),.ce(ce[3]),.d(y3),.q(a)); mux4to1 g4(.d0(r0),.d1(r1),.d2(r2),.d3(4'b0000),.sel(sel),.y(b)); alu a1(.a(a),.b(b),.s(s),.cin(cin),.y(y3)); endmodule </pre>	<pre> module dp_tb; reg[3:0] m0, m1, m2, ce; reg[2:0] w, s; reg[1:0] sel; reg clk, clr, cin; wire [3:0] r0, r1, r2; dp uut(m0, m1, m2, cin, clr, w, ce, sel, s, clk, r0, r1, r2); initial begin clr = 1'b1; w = 3'b000; ce = 4'b0000; sel = 2'b00; s = 3'b000; clk = 1'b0; m2 = 4'b0000; m0 = 4'b0101; m1 = 4'b0011; cin = 1; end always #1 clk = ~clk; initial begin #8; clr = 1'b0; #2; ce = 4'b0011; sel = 2'b00; s = 3'b010; #2; ce = 4'b1011; #2; ce = 4'b0011; sel = 2'b01; s = 3'b001; #2; ce = 4'b1000; #2; ce = 4'b0100; w = 3'b100; #2; w = 3'b000; ce = 4'b0000; sel = 2'b00; s = 3'b000; #8; \$stop; end endmodule </pre>

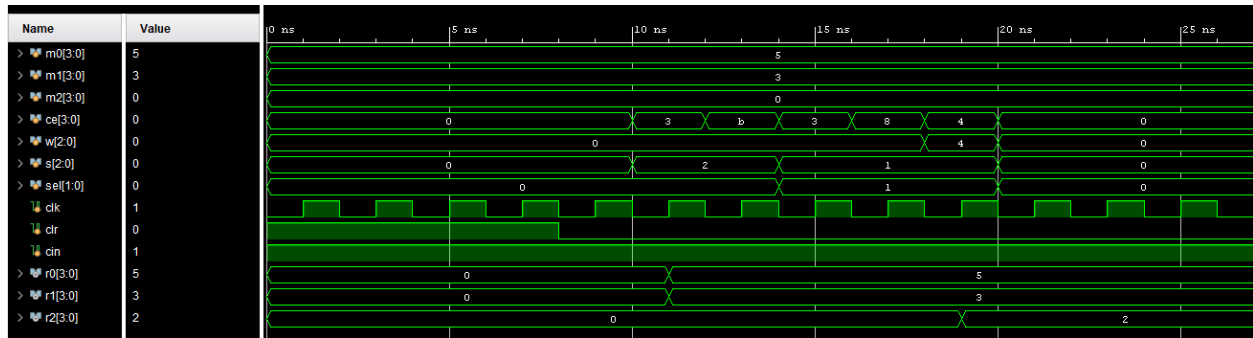

FSM

Source Code	Testbench
<pre> module fsm(clk, reset, clr, w, ce, sel, s); input clk, reset; output reg clr; output reg [2:0] w, s; output reg [1:0] sel; output reg [3:0] ce; reg [2:0] cs, ns; parameter s0=0, s1=1, s2=2, s3=3, s4=4, s5=5; always@(posedge clk or posedge reset) begin if(reset) begin cs <= s0; end else begin cs <= ns; end end always@(cs) begin case(cs) s0 : begin clr = 1'b1; w = 3'b000; s = 3'b000; sel = 2'b00; </pre>	<pre> module fsm_tb; reg clk, reset; wire clr; wire [1:0] sel; wire [2:0] w, s; wire [3:0] ce; fsm uut(clk, reset, clr, ce, w, s, sel); always begin #5 clk = ~clk; end initial begin clk = 0; #2 reset = 1; #10 reset = 0; #150 \$stop; end endmodule </pre>

```
ce = 4'b0000;  
ns <= s1;  
end
```

```
s1 : begin  
clr = 1'b0;  
w = 3'b101;  
s = 3'b000;  
sel = 2'b00;  
ce = 4'b0111;  
ns <= s2;  
end
```

```
s2 : begin  
clr = 1'b0;  
w = 3'b100;  
s = 3'b010;  
sel = 2'b11;  
ce = 4'b1000;  
ns <= s3;  
end
```

```
s3 : begin  
clr = 1'b0;  
w = 3'b100;  
s = 3'b001;  
sel = 2'b10;  
ce = 4'b1000;  
ns <= s4;  
end
```


```
s4 : begin  
clr = 1'b0;  
w = 3'b000;  
s = 3'b000;  
sel = 2'b00;  
ce = 4'b0100;  
ns <= s5;  
end
```

```
s5 : begin  
clr = 1'b0;  
w = 3'b000;  
s = 3'b000;
```

<pre> sel = 2'b00; ce = 4'b0000; ns <= s5; end default : ns = s0; endcase end endmodule </pre>													
<table border="1"> <thead> <tr> <th>Name</th><th>Value</th></tr> </thead> <tbody> <tr><td>clk</td><td>1</td></tr> <tr><td>reset</td><td>0</td></tr> <tr><td>clr</td><td>0</td></tr> <tr><td>> sel[1:0]</td><td>0</td></tr> <tr><td>> w[2:0]</td><td>0</td></tr> </tbody> </table>	Name	Value	clk	1	reset	0	clr	0	> sel[1:0]	0	> w[2:0]	0	
Name	Value												
clk	1												
reset	0												
clr	0												
> sel[1:0]	0												
> w[2:0]	0												

Top

Source Code	Testbench
<pre> module top(sw1, clk, m0, m1, m2, cin, r0, r1, r2); input clk, sw1, cin; input [3:0] m0, m1, m2; output[3:0] r0,r1,r2; wire clr; wire [1:0] sel; wire [2:0] w,s; wire [3:0] ce, r0,r1,r2; fsm g1(.reset(sw1), .clk(clk), .clr(clr), .w(w), .ce(ce), .sel(sel), .s(s)); dp g2(.m0(m0), .m1(m1), .m2(m2), .cin(cin), .clr(clr), .w(w), .ce(ce), .sel(sel), .s(s),.clk(clk), .r0(r0), .r1(r1), .r2(r2)); endmodule </pre>	<pre> module top_tb; reg[3:0] m0,m1,m2,ce; reg[2:0] w,s; reg[1:0] sel; reg sw1, clk, clr, cin; wire [3:0] r0,r1,r2; top utt(sw1, clk, m0, m1, m2, cin, r0, r1, r2); initial begin sw1= 1; clr =1'b1; w= 3'b000; ce= 4'b0000; sel=2'b00; s = 3'b000; clk = 1'b0; m2 = 4'b0000; m0=4'b0000; m1= 4'b0000; cin = 1; end always #1 clk =~clk; initial begin #10; sw1 = 0; #8; clr = 1'b0; #2; ce = 4'b0011; sel = 2'b00; s= 3'b010; #2; ce = 4'b1011; #2; ce = 4'b0011; sel = 2'b01; s= 3'b001; #2; ce = 4'b1011; </pre>

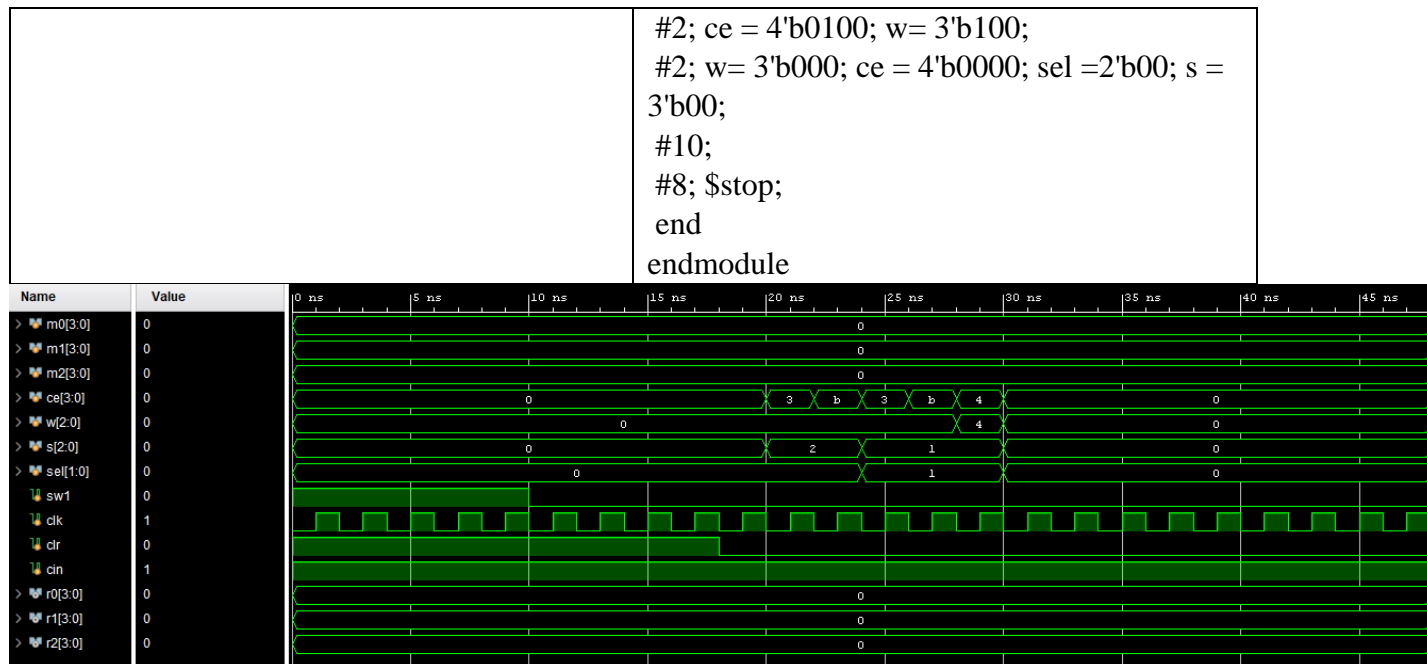

Result Discussion:

The result came out as it should. There was difficulty combining all the coding together since it has been a while since working with Verilog but looking back at old project does help a lot. The only issue I had was logic issue and sometime there might be a mistake in a random while that makes it so the whole file does not work. The testbench at the end also confused me a bit since I overthink to the point where I was confused on what we are testing, but at the end the result came out just fine.

Conclusion:

This part of the lab does sum everything that we learn up till now into one project. This coding requires me to think about the very beginning of the course which was a great thing since I could relearn what was already taught. Each part target specific thing such a fsm, state machine coding, and hierarchy design. Although it was quite difficult to jump back into coding that we have done in a while. I am more familiar with verilog coding compared to HDML coding so I would prefer that over the other. Overall, this lab was helpful in being a reminder of how to code hierarchy along with fsm and state machine.